EE446 Laboratory Project

Single Cycle RISC-V Processor

1. Datapath

 


Figure 1. RTL View of the datapath.

We have designed our datapath described on the Harris & Harris book, but the extended version which includes JAL, JALR, LUI and AUIPC instructions. We also included XORID operation but it did not require us to modify the datapath. We also included Neg and NegU flags from the ALU to have the comparison info from the ALU. We added a mux right before WD3 input of the register file to implement the operations that PC+4 to a register in the register file when there is an operation which writes to PC. Also we extended the PCSrc mux to have 3 inputs. The extra input comes from the ALUResult, which is needed for JALR operation. We extended ALUControl signal to 4 bits to cover all of the ALU operations. You can see the extended and modified datapath from the Harris & Harris book in the next pages. We followed Harris & Harris book for datapath and controller design and did some modifications on it wherever necessary.

Here is an example data flow and control signals for AND instruction.

 


Figure 7.14 Control signals and data flow while executing an and instruction

We extended datapath and controller to include JALR, LUI, AUIPC, BLT, BGE, BLTU, BGEU and XORID operations. Our design does not have ImmSrc as a control signal from the controller but it takes opcode from the instruction and decides on the type of immediate extension depending on the opcode. Here is another implementation on the datapath and controller:

 


Figure 7.15 Enhanced datapath for jal

Table 7.5 ImmSrc encoding.

ImmSrc	ImmExt	Type	Description
00	{{20{Instr[31]}}, Instr[31:20]}	I	12-bit signed immediate
01	{{20{Instr[31]}}, Instr[31:25], Instr[11:7]}	S	12-bit signed immediate
10	{{20{Instr[31]}}, Instr[7], Instr[30:25], Instr[11:8], 1'b0}	В	13-bit signed immediate
11	{{12{Instr[31]}}, Instr[19:12], Instr[20], Instr[30:21], 1'b0}	J	21-bit signed immediate

Figure 2. Extended datapath for JAL instruction.

 


Figure 3. Modified complete datapath from the Harris & Harris book with our additional mux.

2. Controller

 


Figure 4. RTL View of the controller.

We designed the controller in two submodules namely, main decoder and alu decoder and some logic to determine the PCSrc signal. Main decoder creates all the other control signals except ALUControl. ALUControl is created at alu decoder. The data_select signal is for the mux before the WD3 input of the register file. It chooses between PC+4 and result. The other signals are as it is in the design in the book. Neg and NegU are needed and used for Branch instructions, as well as zero. ImmJump is the PCSrc[1] signal which is only asserted in JALR instructions. On the next page you can see a controller which is not complete according to our requirements from the Harris & Harris book.

 


Figure 7.16 Enhanced control unit for jal

Table 7.6 Main Decoder truth table enhanced to support \mathtt{jal}

Instruction	Opcode	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
1 w	0000011	1	00	1	0	01	0	00	0
SW	0100011	0	01	1	1	xx	0	00	0
R-type	0110011	1	XX	0	0	00	0	10	0
beq	1100011	0	10	0	0	XX	1	01	0
I-type ALU	0010011	1	00	1	0	00	0	10	0
jal	1101111	1	11	x	0	10	0	xx	1

3. Testbench

Here you can see the types of operations and their instruction encodings from Harris & Harris book.

31	27	26	25	24		20	19	15	14	12	11	7	6	0	
	funct7				rs2	r		rs1		funct3		$_{ m rd}$		opcode	
imm[11:0]				rs1 f			nct3 rd		opc	code	I-type				
i	mm[11:	5]		rs2		rs1		fun	funct3 imr		n[4:0]	opc	code	S-type	
im	imm[12 10:5] rs2		rs1 funct3		imm[4:1 11]	opc	code	B-type						
	imm[31:12]										1	rd	opc	code	U-type
imm[20 10:1 11 19:12]										1	rd	opc	ode	J-type	

For creating the instructions, we used the list below from the Harris & Harris book:

	imm[31:12]	rd	0110111	LUI		
	imm[31:12]	rd	0010111	AUIPC		
imi	m[20 10:1 11 1]	9:12]		rd	1101111	JAL
imm[11:	0]	rs1	000	rd	1100111	JALR
imm[12 10:5]	rs2	rs1	000	imm[4:1 11]	1100011	BEQ
imm[12 10:5]	rs2	rs1	001	imm[4:1 11]	1100011	BNE
imm[12 10:5]	rs2	rs1	100	imm[4:1 11]	1100011	BLT
imm[12 10:5]	rs2	rs1	101	imm[4:1 11]	1100011	$_{\mathrm{BGE}}$
imm[12 10:5]	rs2	rs1	110	imm[4:1 11]	1100011	BLTU
imm[12 10:5]	rs2	rs1	111	imm[4:1 11]	1100011	BGEU
imm[11:	4	rs1	000	rd	0000011	LB
imm[11:	•	rs1	001	rd	0000011	LH
imm[11:	-	rs1	010	rd	0000011	brack LW
imm[11:	2	rs1	100	rd	0000011	LBU
imm[11:	-	rs1	101	rd	0000011	LHU
imm[11:5]	rs2	rs1	000	imm[4:0]	0100011	brackSB
imm[11:5]	rs2	rs1	001	imm[4:0]	0100011	SH
imm[11:5]	rs2	rs1	010	imm[4:0]	0100011	m SW
		rs1	000			
	imm[11:0]			rd	0010011	ADDI
imm[11:	•	rs1	010	rd	0010011	SLTI
imm[11:		rs1	011	$_{ m rd}$	0010011	SLTIU
imm[11:		rs1	100	rd	0010011	XORI
imm[11:		rs1	110	rd	0010011	ORI
imm[11:		rs1	111	rd	0010011	ANDI
0000000	shamt	rs1	001	rd	0010011	SLLI
0000000	shamt	rs1	101	rd	0010011	SRLI
0100000	shamt	rs1 rs1	101	rd	0010011	SRAI
I	0000000 rs2		000	rd	0110011	ADD
	0100000 rs2		000	rd	0110011	SUB
	0000000 rs2		001	rd	0110011	SLL
0000000			010	rd	0110011	SLT
0000000	I		011	rd	0110011	SLTU
0000000			100	rd	0110011	XOR
0000000			101	rd	0110011	SRL
	0100000 rs2		101 110	rd	0110011	SRA
0000000				rd	0110011	OR
0000000	rs2	rs1	111	rd	0110011	AND

Hilmi Taşkın 2232700 Bilal Yuksu 2110047

Our design can operate all the instructions listed above and XORID instruction that is asked in the project description. The instructions that are used in testbench which cover all the operations in the extended instruction set are below:

93 00 30 01	# addi x1, x0, 0x13
33 81 10 00	# add x2, x1, x1
B3 01 11 40	# sub x3, x2, x1
13 F2 F0 00	# andi x4, x1, 0xF
B3 E2 21 00	# or x5, x3, x2
13 C3 A0 00	# xori x6, x1, 0xA
93 93 20 00	# slli x7, x1, 2
13 54 11 00	# srli x8, x2, 1
93 D4 11 40	# srai x9, x3, 1
13 A5 00 02	# slti x10, x1, 0x10
B3 35 31 00	# sltu x11, x2, x3
63 84 11 00	# beq x1, x3, 0x8
E3 88 30 FE	# beq x1, x3, -16
23 20 10 00	# sw x1, x0, 0
83 25 00 00	# lw x11, x0, 0
23 10 20 00	# sh x2, x0, 0
03 16 00 00	# lh x12, x0, 0
23 00 20 00	# sb x2, x0, 0
83 06 00 00	# lb x13, x0, 0
03 57 00 00	# lhu x14, x0, 0
83 47 00 00	# lbu x15, x0, 0
37 08 00 80	# lui x16, 0x80000
97 88 00 00	# auipc x17, 0x8
EF 08 C0 05	# jal x17, 92
67 89 D0 04	# jalr x18, 77(x1)
8B C9 00 00	# xorid x19, x1

Hilmi Taşkın 2232700 Bilal Yuksu 2110047

For the testbench we used testbench used for ARM Single Cycle Processor and modified it according to our requirements. You can see the testbench code in the code section. The results of the testbench run are below:

Also, you can see how some of the operations are implemented in the performance_model in the testbench:

```
def performance model(self):
   if opcode == 0x33: # R-type
  if funct3 == 0x0:
                self.Register_File[rd] = self.Register_File[rs1] + self.Register_File[rs2]
                self.Register_File[rd] = self.Register_File[rs1] - self.Register_File[rs2]
        elif funct3 == 0x1: # SLL self.Register_File[rs1] << (self.Register_File[rs2] & 0x1F)
        elif funct3
            self.Register_File[rd] = 1 if (self.Register_File[rs1] & 0xFFFFFFFF) < (self.Register_File[rs2] & 0xFFFFFFFF) else 0
        elif funct3
            self.Register_File[rd] = self.Register_File[rs1] ^ self.Register_File[rs2]
        elif funct3 == 0x5:
if funct7 == 0x
            self.Register File[rd] = self.Register File[rs1] | self.Register File[rs2]
   elif opcode == 0x13: # I-type
            self.Register File[rd] = self.Register File[rs1] + imm i
            self.Register_File[rd] = self.Register_File[rs1] << (imm_i & 0x1F)
        elif funct
             self.Register_File[rd] = 1 if self.Register_File[rs1] < imm_i else 0</pre>
```

We implemented the XORID instruction with a xoring the selected register content with the xorid_constant which is the xor of the student ids of us. You can also see the some different instruction types below:

```
C: > Users > Msi > OneDrive > Belgeler > risc-v_test > Test > ♥ RISC-V_Test.py > ...
            def performance model(self):
                     if funct3 == 0x0: #
                        if self.Register_File[rs1] == self.Register_File[rs2]:
                        if self.Register_File[rs1] != self.Register_File[rs2]:
                              self.PC += imm b
                               self.PC += imm_b
                     elif funct3 == 0x5: #
                        if self.Register_File[rs1] >= self.Register_File[rs2]:
                               self.PC += imm_b
                     elif funct3 == 0x6:
                               self.PC += imm b
                         if (self.Register_File[rs1] & 0xFFFFFFFF) >= (self.Register_File[rs2] & 0xFFFFFFFF):
                              self.PC += imm b
                elif opcode == 0x6F: # J-type
self.Register_File[rd] = self.PC + 4
                     self.PC = imm i
                elif opcode == 0x67: # I-type for JALR
    self.Register_File[rd] = self.PC + 4
                     self.PC = (self.Register_File[rs1] + imm_i) & ~1
                elif opcode == 0x37: # U-type LUI
    self.Register_File[rd] = imm_u
                elif opcode == 0x17: # U-type AUIPC
    self.Register_File[rd] = self.PC + 4
```